

## Multiplication

37

### Multiplication of Unsigned Numbers

- Multiplication requires substantially more hardware than addition.
- Multiplication of two  $n$ -bit number generates a  $2n$ -bit product.
- We can use shift-and-add method.
  - Repeated additions of shifted versions of the multiplicand.

1 0 1 0	<b>Multiplicand M</b>	<b>(10)</b>
1 1 0 1	<b>Multiplier Q</b>	<b>(13)</b>
-----		
1 0 1 0		
0 0 0 0		
1 0 1 0		
1 0 1 0		
-----		
1 0 0 0 0 0 1 0	<b>Product P</b>	<b>(130)</b>

38

38

## A General Case

$$\begin{array}{r}
 \begin{array}{cccc}
 A_3 & A_2 & A_1 & A_0 \\
 B_3 & B_2 & B_1 & B_0
 \end{array} \\
 \hline
 \begin{array}{cccc}
 A_3B_0 & A_2B_0 & A_1B_0 & A_0B_0 \\
 A_3B_1 & A_2B_1 & A_1B_1 & A_0B_1 \\
 A_3B_2 & A_2B_2 & A_1B_2 & A_0B_2 \\
 A_3B_3 & A_2B_3 & A_1B_3 & A_0B_3
 \end{array} \\
 \hline
 \end{array}$$


- Each  $A_iB_j$  is called a *partial product*.
- Generating the partial products is easy.
  - Requires just an AND gate for each partial product.
- Adding all the  $n$ -bit partial products in hardware is more difficult.

39

39
 
## Design of a Combinational Array Multiplier

- We can directly map the multiplication process as discussed to hardware.
  - We use an array of cells to generate the partial products.
  - Instead of adding the partial products at the end, we add the partial products at every stage of the multiplication.
- The required multiplication cell is as shown.
  - Combines capabilities of partial product generation and also addition of partial products.




40

40

- Extremely inefficient, and requires very large amount of hardware.
- Requires  $n^2$  multiplication cells for an  $n \times n$  multiplier.
- Advantage is that it is very fast.
 
$$\begin{array}{cccc}
 m_3 & m_2 & m_1 & m_0 \\
 q_3 & q_2 & q_1 & q_0 \\
 \hline
 m_3q_0 & m_2q_0 & m_1q_0 & m_0q_0 \\
 m_3q_1 & m_2q_1 & m_1q_1 & m_0q_1 \\
 m_3q_2 & m_2q_2 & m_1q_2 & m_0q_2 \\
 m_3q_3 & m_2q_3 & m_1q_3 & m_0q_3 \\
 \hline
 \end{array}$$



product:  $p_7 p_6 p_5 p_4 p_3 p_2 p_1 p_0$

41

41

## Unsigned Sequential Multiqlication

- Requires much less hardware, but requires several clock cycles to perform multiplication of two  $n$ -bit numbers.
  - Typical hardware complexity:  $O(n)$
  - Typical time complexity:  $O(n)$
- In the “*hand multiplication*” that we have seen:
  - If the  $i$ -th bit of the multiplier is **1**, the multiplicand is shifted left by  $i$  bit positions, and added to the partial product.
  - The relative position of the partial products do not change; it is the multiplicand that gets shifted left.


42

42

- In the “*shift-and-add*” multiplication that we discuss now, we make the following modifications.
  - We do not shift the multiplicand (i.e., keep its position fixed).
  - We right shift an *2n*-bit partial product at every step.

43

43

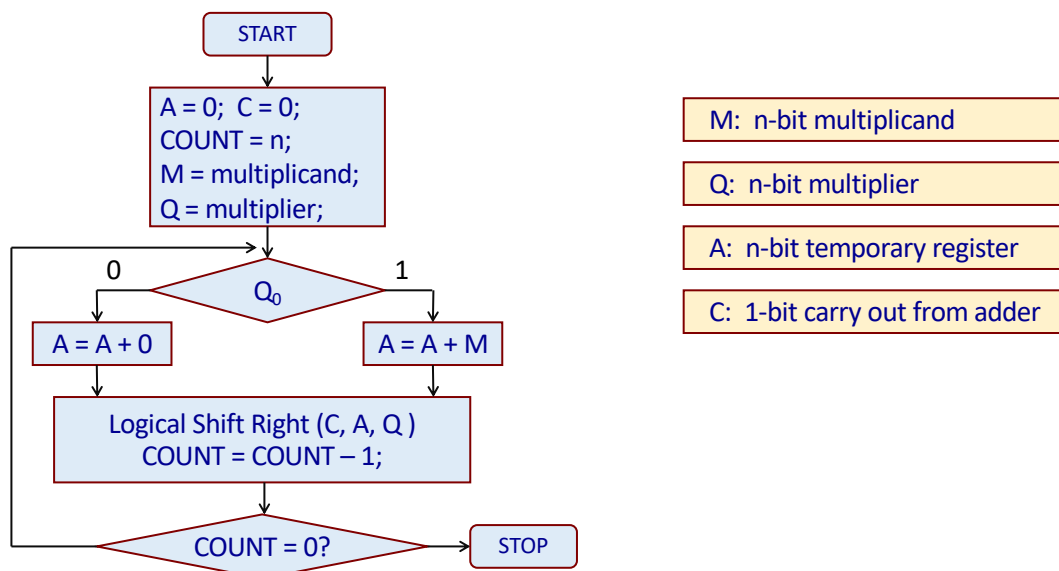

44

44

**Example 1:**  $(10) \times (13)$ 

Assume 5-bit numbers.

M:  $(01010)_2$ Q:  $(01101)_2$ 

product = 130

 $= (0010000010)_2$ 

C	A	Q		
0	0 0 0 0 0	0 1 1 0 <b>1</b>	Initialization	
0	0 1 0 1 0	0 1 1 0 1	$A = A + M$	Step 1
0	0 0 1 0 1	0 0 1 1 <b>0</b>	Shift	
0	0 0 1 0 1	0 0 1 1 0	$A = A + 0$	Step 2
0	0 0 0 1 0	1 0 0 1 <b>1</b>	Shift	
0	0 1 1 0 0	1 0 0 1 1	$A = A + M$	Step 3
0	0 0 1 1 0	0 1 0 0 <b>1</b>	Shift	
0	1 0 0 0 0	0 1 0 0 1	$A = A + M$	Step 4
0	0 1 0 0 0	0 0 1 0 <b>0</b>	Shift	
0	0 1 0 0 0	0 0 1 0 0	$A = A + 0$	Step 5
0	0 0 1 0 0	0 0 0 1 0	Shift	

45

45

**Example 2:**  $(29) \times (21)$ 

Assume 5-bit numbers.

M:  $(11101)_2$ Q:  $(10101)_2$ 

product = 609


 $= (1001100001)_2$ 

C	A	Q		
0	0 0 0 0 0	1 0 1 0 <b>1</b>	Initialization	
0	1 1 1 0 1	1 0 1 0 1	$A = A + M$	Step 1
0	0 1 1 1 0	1 1 0 1 <b>0</b>	Shift	
0	0 1 1 1 0	1 1 0 1 0	$A = A + 0$	Step 2
0	0 0 1 1 1	0 1 1 0 <b>1</b>	Shift	
1	0 0 1 0 0	0 1 1 0 1	$A = A + M$	Step 3
0	1 0 0 1 0	0 0 1 1 <b>0</b>	Shift	
0	1 0 0 1 0	0 0 1 1 0	$A = A + 0$	Step 4
0	0 1 0 0 1	0 0 0 1 <b>1</b>	Shift	
1	0 0 1 1 0	0 0 0 1 1	$A = A + M$	Step 5
0	1 0 0 1 1	0 0 0 0 1	Shift	

46

46
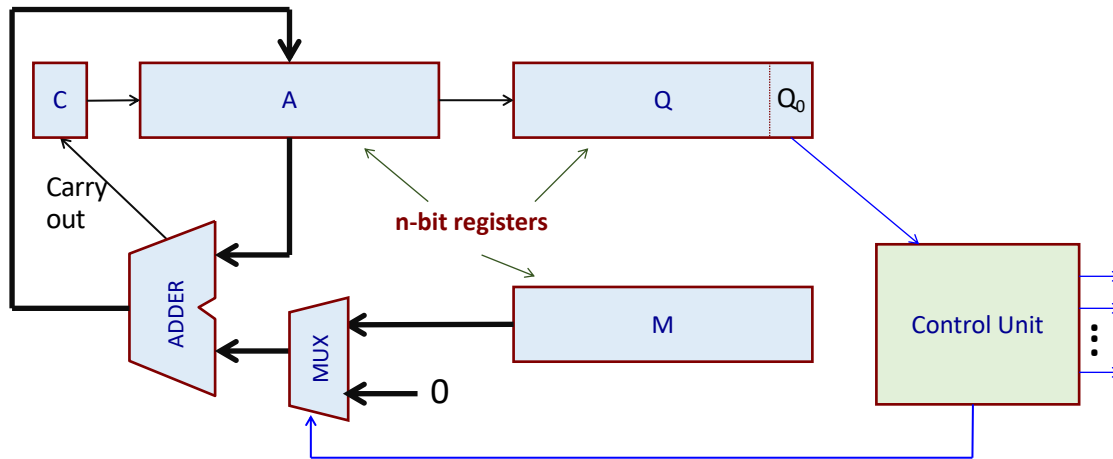
### Data path for Shift-and-Add Multiplier



47

47

### Signed Multiplication

- We can extend the basic shift-and-add multiplication method to handle signed numbers.
- One important difference:
  - Require to sign-extend all the partial products before they are added.
  - Recall that for 2's complement representation, sign extension can be done by replicating the sign bit any number of times.

0101 = 0000 0101 = 0000 0000 0000 0101 = 0000 0000 0000 0000 0000 0000 0000 0101

1011 = 1111 1011 = 1111 1111 1111 1011 = 1111 1111 1111 1111 1111 1111 1111 1011

48

48

## An Example: 6-bit 2's complement multiplication

Note: For  $n$ -bit multiplication, since we are generating a  $2n$ -bit product, overflow can never occur.

```

      1 1 0 1 0 1      (-11)
    x 0 1 1 0 1 0      (+26)
-----
0 0 0 0 0 0 0 0 0 0 0 0
1 1 1 1 1 1 1 0 1 0 1
0 0 0 0 0 0 0 0 0 0
1 1 1 1 1 0 1 0 1
1 1 1 1 0 1 0 1
0 0 0 0 0 0 0
-----
1 1 1 0 1 1 1 0 0 0 1 0      (-286)

```

49

49

## Booth's Algorithm for Signed Multiplication

- In the conventional shift-and-add multiplication as discussed, for  $n$ -bit multiplication, we iterate  $n$  times.
  - Add either 0 or the multiplicand to the  $2n$ -bit partial product (depending on the next bit of the multiplier).
  - Shift the  $2n$ -bit partial product to the right.
- Essentially we need  $n$  additions and  $n$  shift operations.
- Booth's algorithm is an improvement whereby we can avoid the additions whenever consecutive 0's or 1's are detected in the multiplier.
  - Makes the process faster.

50

50

## Basic Idea Behind Booth's Algorithm

- We inspect two bits of the multiplier ( $Q_i, Q_{i-1}$ ) at a time.
  - If the bits are same (00 or 11), we only shift the partial product.
  - If the bits are 01, we do an addition and then shift.
  - If the bits are 10, we do a subtraction and then shift.
- Significantly reduces the number of additions / subtractions.
- Inspecting bit pairs as mentioned can also be expressed in terms of *Booth's Encoding*.
  - Use the symbols +1, -1 and 0 to indicate changes w.r.t.  $Q_i$  and  $Q_{i-1}$ .
  - $01 \rightarrow +1$ ,  $10 \rightarrow -1$ , 00 or 11  $\rightarrow 0$ .
  - For encoding the least significant bit  $Q_0$ , we assume  $Q_{-1} = 0$ .

51

51


- Examples of Booth encoding:
 

a)	0 1 1 1 0 0 0 0 ::	+1 0 0 -1 0 0 0 0
b)	0 1 1 1 0 1 1 0 ::	+1 0 0 -1 +1 0 -1 0
c)	0 0 0 0 0 1 1 1 ::	0 0 0 0 +1 0 0 -1
d)	0 1 0 1 0 1 0 1 ::	+1 -1 +1 -1 +1 -1 +1 -1
- The last example illustrates the *worst case* for Booth's multiplication (alternating 0's and 1's in multiplier).
  - In the illustrations, we shall show the two multiplier bits explicitly instead of showing the encoded digits.

52

52



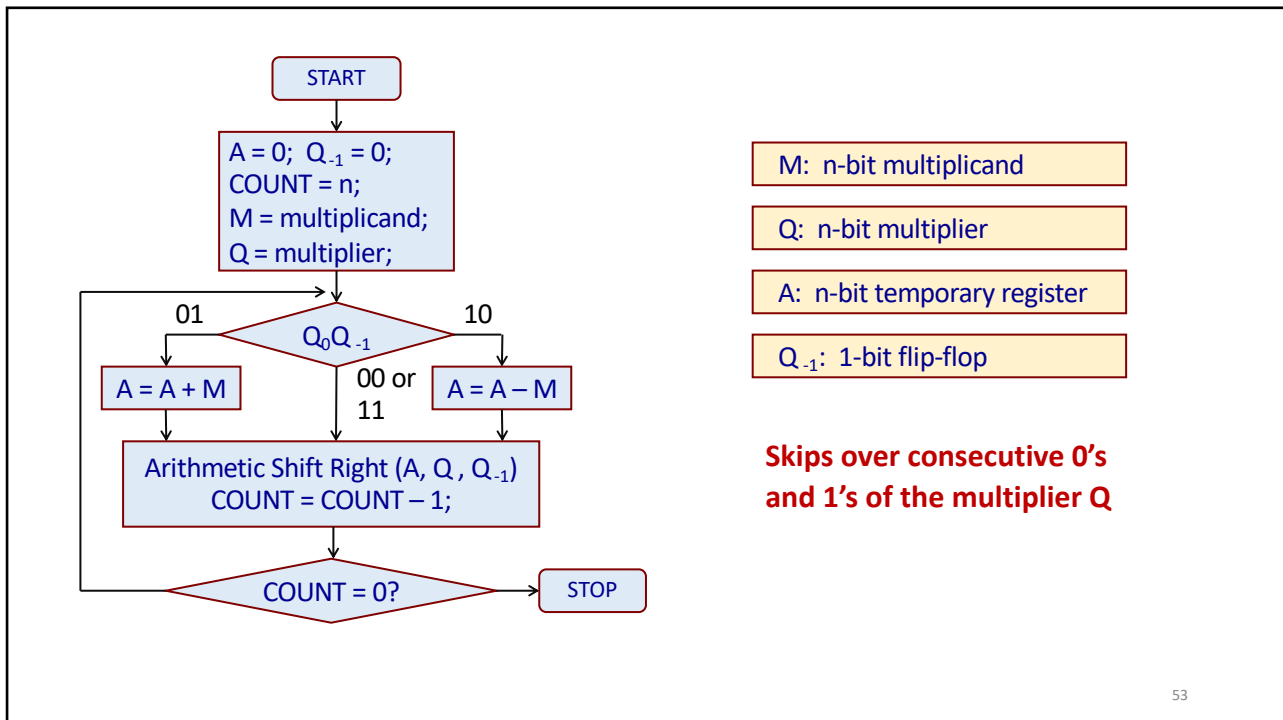

53

<b>Example 1:</b> $(-10) \times (13)$ Assume 5-bit numbers. M: $(10110)_2$ -M: $(01010)_2$ Q: $(01101)_2$ product = -130 = $(1101111110)_2$	<b>A</b>	<b>Q</b>	<b>Q<sub>-1</sub></b>		
	0 0 0 0 0	0 1 1 0	1 0	Initialization	
	0 1 0 1 0	0 1 1 0 1	0	A = A - M	Step 1
	0 0 1 0 1	0 0 1 1	0 1	Shift	
	1 1 0 1 1	0 0 1 1 0	1	A = A + M	Step 2
	1 1 1 0 1	1 0 0 1	1 0	Shift	
	0 0 1 1 1	1 0 0 1 1	0	A = A - M	Step 3
	0 0 0 1 1	1 1 0 0	1 1	Shift	
	0 0 0 0 1	1 1 1 1	0 1	Shift	Step 4
	1 0 1 1 1	1 1 1 0 0	1	A = A + M	Step 5
	1 1 0 1 1	1 1 1 1 0	0	Shift	

54

**Example 2:**

$$(-31) \times (28)$$

Assume 6-bit numbers.

$$M: (100001)_2$$

$$-M: (011111)_2$$

$$Q: (011100)_2$$

$$\text{product} = -868$$

$$= (110010011100)_2$$


A	Q	Q <sub>-1</sub>		
0 0 0 0 0 0	0 1 1 1 0	0 0	Initialization	
0 0 0 0 0 0	0 0 1 1 1	0 0	Shift	Step 1
0 0 0 0 0 0	0 0 0 1 1	1 0	Shift	Step 2
0 1 1 1 1 1	0 0 0 1 1	1 0	A = A - M	Step 3
0 0 1 1 1 1	1 0 0 0 1	1 1	Shift	
0 0 0 1 1 1	1 1 0 0 0	1 1	Shift	Step 4
0 0 0 0 1 1	1 1 1 0 0	0 1	Shift	Step 5
1 0 0 1 0 0	1 1 1 0 0 0	1	A = A + M	Step 6
1 1 0 0 1 0	0 1 1 1 0 0	0	Shift	

55

55

**Data path for Booth's Algorithm**

Arithmetic  
shift right

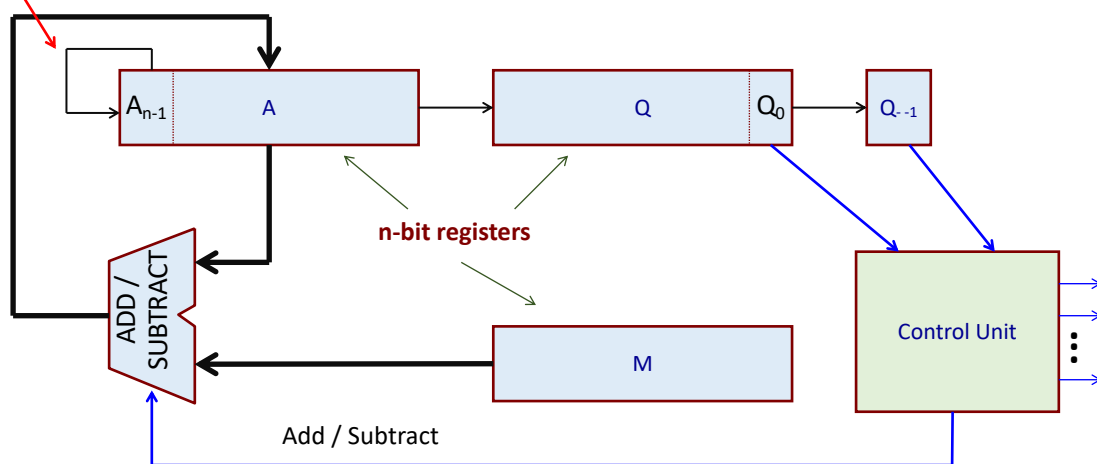

56

56

## Design of Fast Multiplier

### a) Bit-pair Recoding of Booth's Multiplication

- A technique that halves the maximum number of summands; derived directly from the Booth's algorithm.
- If we group the Booth-coded multiplier digits in pairs, we observe:
  - (+1, -1):  $(+1, -1) * M = 2 * M - M = M$
  - (0, +1):  $(0, +1) * M = M$
- We need a single addition instead of a pair of addition & subtraction.
  - Other similar rules can be framed.
  - Shown on next slide.

57

57

Original Booth-coded pair	Equivalent Recoded pair
(+1, 0)	(0, +2)
(-1, +1)	(0, -1)
(0, 0)	(0, 0)
(0, 1)	(0, 1)
(+1, 1)	--
(+1, -1)	(0, +1)
(-1, 0)	(0, -2)

- Every equivalent recoded pair has at least one 0.
- Worst-case number of additions or subtractions is 50% of the number of multiplier bits.
- Reduces the worst-case time required for multiplication.

58

58

**Example:** (+13) X (-22) in 6-bits.

Original: Multiplier -- 1 0 1 0 1 0  
 Booth: Multiplier -- -1 +1 -1 +1 -1 0  
 Recoded: Multiplier -- 0 -1 0 -1 0 -2

```

      0 0 1 1 0 1
      . -1 . -1 . -2
-----
  1 1 1 1 1 1 1 0 0 1 1 0
  1 1 1 1 1 1 0 0 1 1
  1 1 1 1 0 0 1 1
-----
  1 1 0 1 1 1 1 0 0 0 1 0

```

- $M = 001101 (+13)$
- $-1 * M = 110011$
- $-2 * M = 100110$

59

59

### b) Carry Save Multiplier

- We have seen earlier how carry save adders (CSA) can be used to add several numbers with carry propagation only in the last stage.
- The partial products can be generated in parallel using  $n^2$  AND gates.
- The  $n$  partial products can then be added using a CSA tree.
- Instead of letting the carries ripple through during addition, we *save* them and feed it to the next row, at the correct weight positions.

```


      m3  m2  m1  m0
      q3  q2  q1  q0
-----
      m3q0 m2q0 m1q0 m0q0
      m3q1 m2q1 m1q1 m0q1
      m3q2 m2q2 m1q2 m0q2
      m3q3 m2q3 m1q3 m0q3
-----

```

60

60

## 4 x 4 Carry Save Multiplier

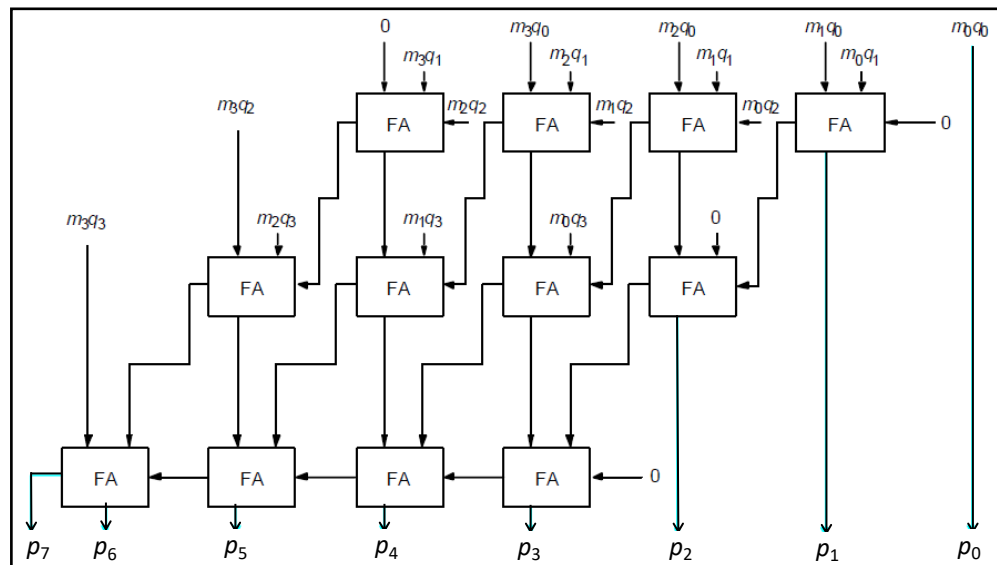

61

61


### • Wallace Tree Multiplier

- A Wallace tree is a circuit that reduces the problem of summing  $n$   $n$ -bit numbers to the problem of summing two  $\Theta(n)$ -bit numbers.
- It uses  $n/3$  (floor of) carry-save adders in parallel to convert the sum of  $n$  numbers to the sum of  $2n/3$  (ceiling of) numbers.
- It then recursively constructs a Wallace tree on the  $2n/3$  (ceiling of) resulting numbers.
- The set of numbers is progressively reduced until there are only two numbers left.
- By performing many carry-save additions in parallel, Wallace trees allow two  $n$ -bit numbers to be multiplied in  $\Theta(\log_2 n)$  time using a circuit of size  $\Theta(n^2)$ .

62

62

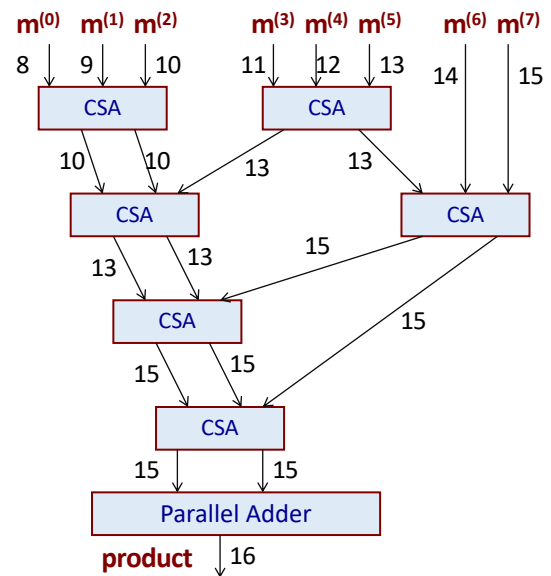- The figure shows a Wallace tree that adds 8 partial products  $m^{(0)}, m^{(1)}, \dots, m^{(7)}$ .
- The partial product  $m^{(i)}$  consists of  $(n + i)$  bits.
- Each line represents an entire number – the label of an edge indicates the number of bits.
- The carry-lookahead adder at the bottom adds two  $(2n-1)$ -bit numbers to give the  $2n$ -bit product.



63

63

## Division

64

## Introduction

- Division is more complex than multiplication.
- Example: Typical values in Pentium-3 processor →
  - Not easy to construct high-speed dividers.
- The ratios have not changed much in later processors.

Instruction	Latency	Cycles / Issue
Load / Store	3	1
Integer Multiply	4	1
Integer Divide	36	36
Floating-point Add	3	1
Floating-point Multiply	5	2
Floating-point Divide	38	38

65

65

- **Latency:**

- Minimum delay after which the first result is obtained, starting from the time when the first set of inputs is applied.

- **Cycles/Issue:**

- Whenever a new set of inputs is applied to a functional unit (e.g. adder), it is called an *issue*.
- Pipelined implementation of arithmetic unit reduces the number of clock cycles between successive issues.
- For non-pipelined arithmetic units (e.g. divider), the number of clock cycles between successive issues is much higher.
  - Next input can be applied only after the previous operation is complete.

66

66

## The Process of Integer Division

- In integer division, a *divisor*  $M$  and a *dividend*  $D$  are given.
- The objective is to find a third number  $Q$ , called the *quotient*, such that
 
$$D = Q \times M + R$$
 where  $R$  is the *remainder* such that  $0 \leq R < M$ .
- The relationship  $D = Q \times M$  suggests that there is a close correspondence between division and multiplication.
  - Dividend, quotient and divisor correspond to product, multiplicand and multiplier, respectively.
  - Similar algorithms and circuits can be used for multiplication and division.

67

67

- One of the simplest division methods is the sequential digit-by-digit algorithm similar to that used in pencil-and-paper methods.

<div style="border: 1px solid red; padding: 5px; width: fit-content;"> <math>D = 37 = (100101)_2</math>  <math>M = 6 = (110)_2</math>            Quotient <math>Q = 6</math>            Remainder <math>R = 1</math> </div>	<div style="display: flex; align-items: center;"> <div style="margin-right: 10px;">Divisor <math>M</math></div> <div style="border-left: 1px solid black; padding-left: 10px;"> <div style="text-align: right; margin-bottom: 5px;"><math>0\ 1\ 1\ 0</math></div> <div style="text-align: right; margin-bottom: 5px;"><math>1\ 0\ 0\ 1\ 0\ 1</math></div> <div style="text-align: right; margin-bottom: 5px;"><math>1\ 1\ 0</math></div> <div style="border-top: 1px dashed black; margin-bottom: 5px;"></div> <div style="text-align: right; margin-bottom: 5px;"><math>1\ 0\ 0\ 1\ 0\ 1</math></div> <div style="text-align: right; margin-bottom: 5px;"><math>- \ 1\ 1\ 0</math></div> <div style="border-top: 1px dashed black; margin-bottom: 5px;"></div> <div style="text-align: right; margin-bottom: 5px;"><math>0\ 1\ 1\ 0\ 1</math></div> <div style="text-align: right; margin-bottom: 5px;"><math>- \ 1\ 1\ 0</math></div> <div style="border-top: 1px dashed black; margin-bottom: 5px;"></div> <div style="text-align: right; margin-bottom: 5px;"><math>0\ 0\ 0\ 1</math></div> <div style="text-align: right; margin-bottom: 5px;"><math>1\ 1\ 0</math></div> <div style="border-top: 1px dashed black; margin-bottom: 5px;"></div> <div style="text-align: right;"><math>0\ 0\ 1</math></div> </div> </div>	Quotient $Q = Q_0Q_1Q_2Q_3$ Dividend $D = R_0$ $Q_0 \cdot M$ ( <i>Does not go; <math>Q_0 = 0</math></i> )  $R_1$ $Q_1 \cdot 2^{-1} \cdot M$ ( <i>Does go; <math>Q_1 = 1</math></i> )  $R_2$ $Q_2 \cdot 2^{-2} \cdot M$ ( <i>Does go; <math>Q_2 = 1</math></i> )  $R_3$ $Q_3 \cdot 2^{-3} \cdot M$ ( <i>Does not go; <math>Q_3 = 0</math></i> )  $R_4 = \text{Remainder } R$
---	---	--

68

68



- In the example, the quotient  $Q = Q_0Q_1Q_2\dots$  is computed one bit at a time.
  - At each step  $i$ , the divisor shifted  $i$  bits to the right (i.e.  $2^{-i} \cdot M$ ) is compared with the current partial remainder  $R_i$ .
  - The quotient bit  $Q_i$  is set to 0 (1) if  $2^{-i} \cdot M$  is greater than (less than)  $R_i$ .
  - The new partial remainder  $R_{i+1}$  is computed as:

$$R_{i+1} = R_i - Q_i \cdot 2^{-i} \cdot M$$

69

69

- **Machine implementation:**

- For hardware implementation, it is more convenient to shift the partial remainder to the left relative to a fixed divisor; thus

$$R_{i+1} = 2R_i - Q_i \cdot M \quad (\text{instead of } R_{i+1} = R_i - Q_i \cdot 2^{-i} \cdot M)$$

- The final partial remainder is the required remainder shifted to the left, so that  $R = 2^{-3} \cdot R_4$  (see next slide).

70

70

Divisor M		Dividend = $2R_0$	Quotient Q
1 1 0	1 0 0 1 0 1	$Q_0 \cdot M$	0
	<b>1 1 0</b>	-----	
	1 0 0 1 0 1 $R_1$		
	1 0 0 1 0 1 0 $2R_1$		
	1 1 0 $Q_1 \cdot M$	-----	0 1
	0 1 1 0 1 0 $R_2$		
	0 1 1 0 1 0 0 $2R_2$		
	1 1 0 $Q_2 \cdot M$	-----	0 1 1
	0 0 0 1 0 0 $R_3$		
	0 0 0 1 0 0 0 $2R_3$		
	<b>1 1 0</b> $Q_3 \cdot M$	-----	0 1 1 0
	0 0 1 0 0 0 $R_4 = 2^3 \cdot R$		

**Do not subtract**

$D = 37 = (100101)_2$   
 $M = 6 = (110)_2$   
 Quotient  $Q = 6$   
 Remainder  $R = 1$

71


71

## Two alternatives approaches for division

- We shall discuss two approaches:
  - a) Restoring division
  - b) Non-restoring division

72
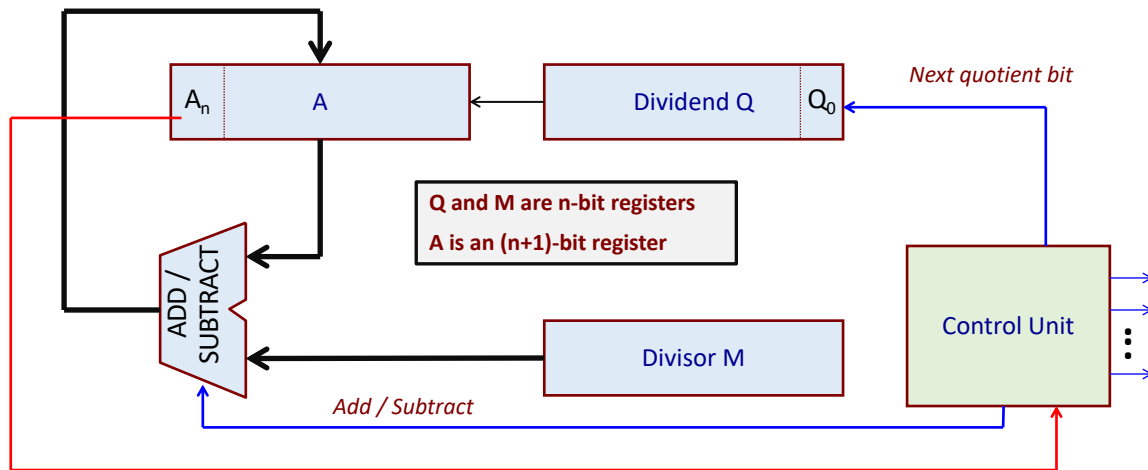
### (a) Restoring Division: The Data Path




73

73
 
### Basic Steps (Restoring Division)


Repeat the following steps  $n$  times:

- Shift the dividend left one bit at a time into register  $A$ .
- Subtract the divisor  $M$  from this register  $A$  (*trial subtraction*).
- If the result is negative (*i.e. not going*):
  - Add the divisor  $M$  back into the register  $A$  (*i.e. restoring back*).
  - Record **0** as the next quotient bit.
- If the result is positive:
  - Do not restore the intermediate result.
  - Record **1** as the next quotient bit.



74

74

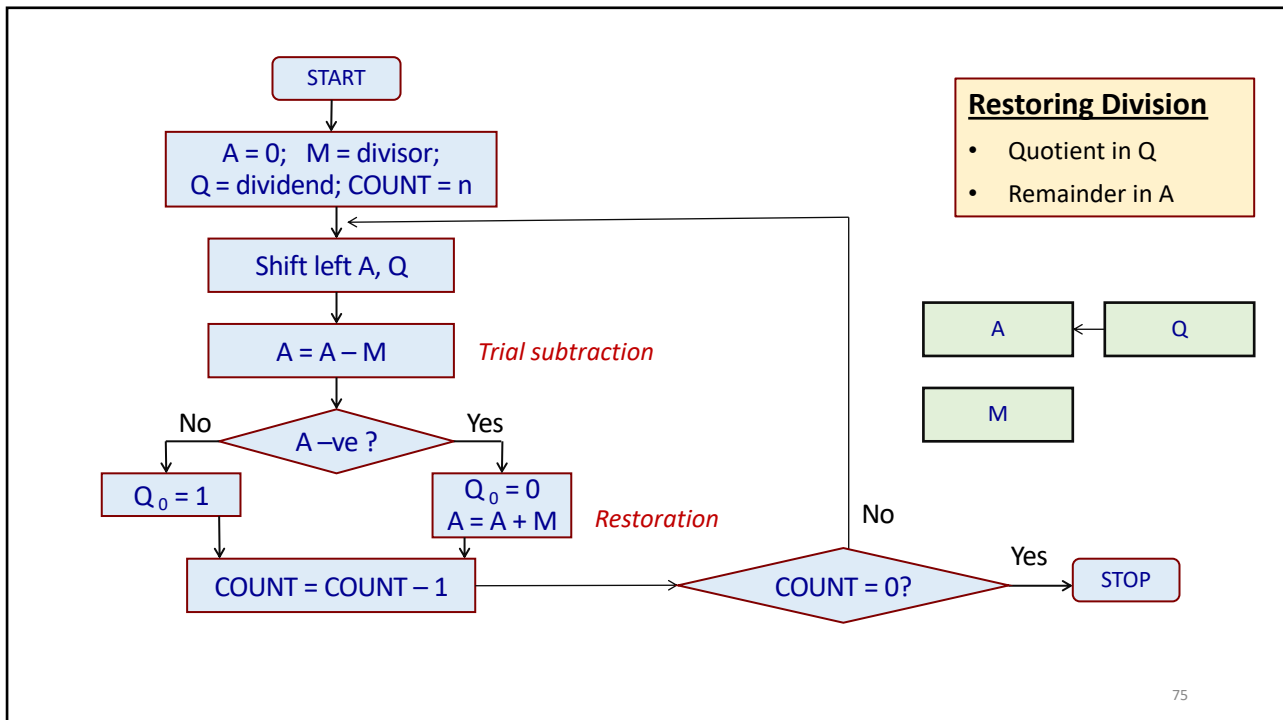

75

#### • Analysis:

- For  $n$ -bit divisor and  $n$ -bit dividend, we iterate  $n$  times.
- Number of trial subtractions:  $n$
- Number of restoring additions:  $n/2$  on the average
  - Best case:  $0$
  - Worst case:  $n$

76

76

### A Simple Example: 8/3 for 4-bit representation (n=4)

Initially:	0 0 0 0 0	1 0 0 0
Shift:	0 0 0 0 1	0 0 0 -
Subtract:	0 0 1 1	
Set $Q_0$ :	1 1 1 1 0	
Restore:	0 0 1 1	
	0 0 0 0 1	0 0 0 0
Shift:	0 0 0 1 0	0 0 0 -
Subtract:	0 0 1 1	
Set $Q_0$ :	1 1 1 1 1	
Restore:	0 0 1 1	
	0 0 0 1 0	0 0 0 0

Shift:	0 0 1 0 0	0 0 0 -
Subtract:	0 0 1 1	
Set $Q_0$ :	0 0 0 0 1	
	0 0 0 0 0	0 0 0 1
Shift:	0 0 0 1 0	0 0 1 -
Subtract:	0 0 1 1	
Set $Q_0$ :	1 1 1 1 1	
Restore:	0 0 1 1	
	0 0 0 1 0	0 0 1 0


Remainder  
00010 = 2

Quotient  
0010 = 2

77

77

### (b) Non-Restoring Division

 

- The performance of restoring division algorithm can be improved by exploiting the following observation.
- In restoring division, what we do actually is:
  - If  $A$  is positive, we shift it left and subtract  $M$ .
    - That is, we compute  $2A - M$ .
  - If  $A$  is negative, we restore it by doing  $A + M$ , shift it left, and then subtract  $M$ .
    - That is, we compute  $2(A + M) - M = 2A + M$ .
- We can accordingly modify the basic division algorithm by eliminating the restoring step → **NON-RESTORING DIVISION**.

Shift left means  
multiplying by 2.

78

78


• **Basic steps in non-restoring division:**

- Start by initializing register  $A$  to 0, and repeat steps (b)-(d)  $n$  times.
- If the value in register  $A$  is positive,
  - Shift  $A$  and  $Q$  left by one bit position.
  - Subtract  $M$  from  $A$ .
- If the value in register  $A$  is negative,
  - Shift  $A$  and  $Q$  left by one bit position.
  - Add  $M$  to  $A$ .
- If  $A$  is positive, set  $Q_0 = 1$ ; else, set  $Q_0 = 0$ .
- If  $A$  is negative, add  $M$  to  $A$  as a final corrective step.

79

79

79


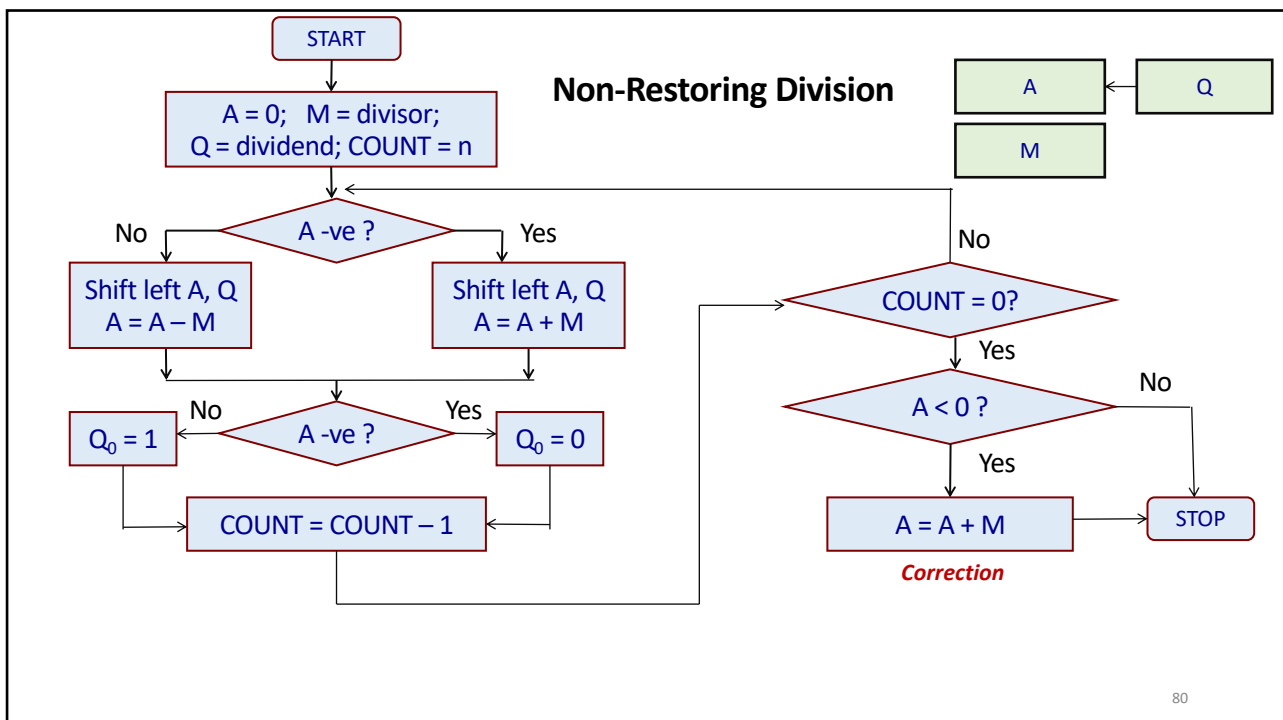


80

80

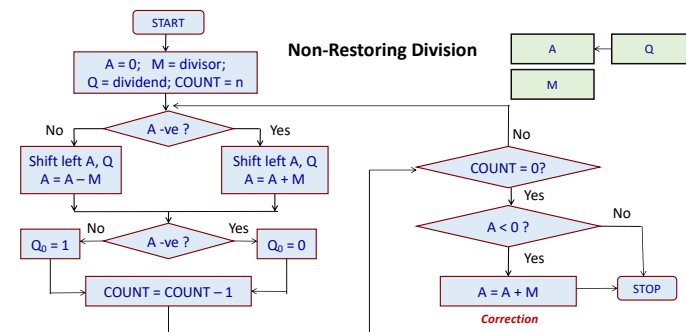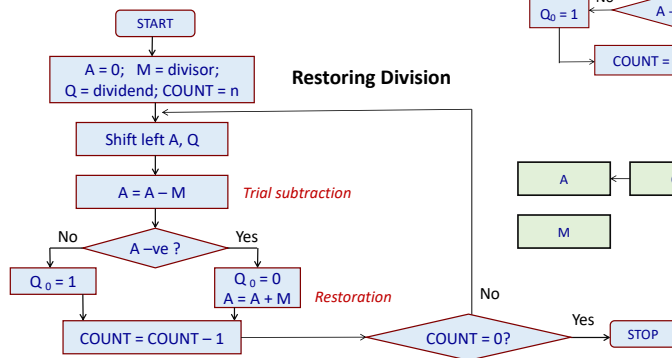**Restoring Division:**

- If  $A$  is positive, we shift it left and subtract  $M$ . That is, we compute  $2A - M$ .
- If  $A$  is negative, we restore is by doing  $A + M$ , shift it left, and then subtract  $M$ . That is, we compute  $2(A + M) - M = 2A + M$ .



81

**A Simple Example: 8/3 for n=4**

Initially: 0 0 0 0 0 1 0 0 0

Shift: 0 0 0 0 1 0 0 0 -

Subtract: - 0 0 1 1

Set Q<sub>0</sub>: 1 1 1 1 0 0 0 0 0

Shift: 1 1 1 0 0 0 0 0 -

Add: 0 0 1 1

Set Q<sub>0</sub>: 1 1 1 1 1 0 0 0 0

Shift: 1 1 1 1 0 0 0 0 -

Add: 0 0 1 1

Set Q<sub>0</sub>: 0 0 0 0 1 0 0 0 1

Shift: 0 0 0 1 0 0 0 1 -

Subtract: - 0 0 1 1

Set Q<sub>0</sub>: 1 1 1 1 0 0 0 1 0

Correction Add:

1 1 1 1 1

0 0 0 1 1


0 0 0 1 0

**Quotient**  
**0010 = 2****Remainder**  
**00010 = 2**

82

82

### Data Path for Non-Restoring Division

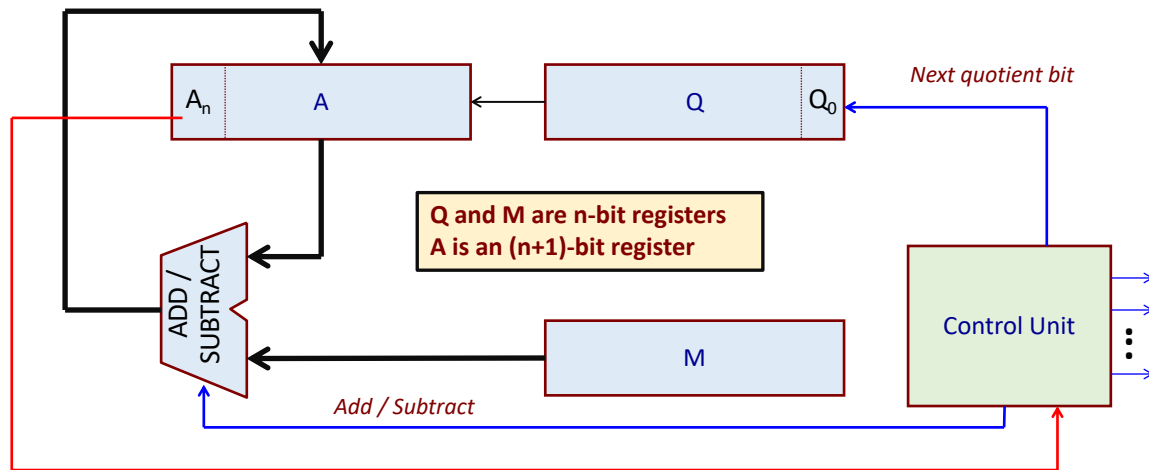

83

83

### High Speed Dividers

- Some of the methods used to increase the speed of multiplication can also be modified to speed up division.
  - High-speed addition and subtraction.
  - High-speed shifting.
  - Combinational array divider (implementing restoring division).
- The main difficulty is that it is very difficult to implement division in a pipeline to improve the performance.
  - Unlike multiplication, where carry-save Wallace tree multipliers can be used for pipeline implementation.

84

84