

Computer Organization and Architecture

Module 6

Computer Arithmetic

Prof. Indranil Sengupta

Dr. Sarani Bhattacharya

Department of Computer Science and Engineering

IIT Kharagpur

Computer Arithmetic

Introduction

- Computers are built using tiny electronic switches.
 - Typically made up of MOS transistors.
 - The state of the switches are typically expressed in binary (ON/OFF).
- To design arithmetic circuits for use in computers, we need to work with *binary numbers*.
 - How to carry out various arithmetic operations in binary?
 - How to implement them efficiently in hardware?


Addition / Subtraction

Addition of Two Binary Digits (Bits)

- When two bits A and B are added, a sum (S) and carry (C) are generated as per the following truth table:

Inputs		Outputs	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

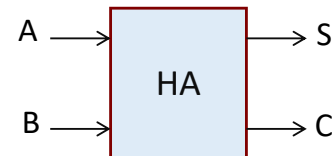
$0 + 0 = 00$
 $0 + 1 = 01$
 $1 + 0 = 01$
 $1 + 1 = 10$



HALF ADDER

$$S = A'.B + A.B' = A \oplus B$$

$$C = A.B$$

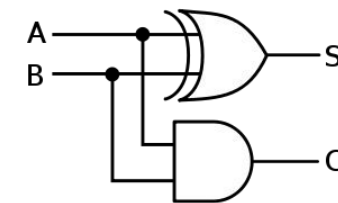

Addition of Multi-bit Binary Numbers

$$\begin{array}{r} 0010110 \leftarrow \text{Carry} \\ 0101011 \leftarrow \text{Number A} \\ + 0001001 \leftarrow \text{Number B} \\ \hline 0110100 \leftarrow \text{Sum S} \end{array}$$

$$\begin{array}{r} 1111110 \leftarrow \text{Carry} \\ 0111111 \leftarrow \text{Number A} \\ + 0000001 \leftarrow \text{Number B} \\ \hline 1000000 \leftarrow \text{Sum S} \end{array}$$


- At every bit position (stage), we require to add 3 bits:

- 1 bit for number A
- 1 bit for number B
- 1 carry bit coming from the previous stage

WE NEED A FULL ADDER

Full Adder

Inputs			Outputs	
A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

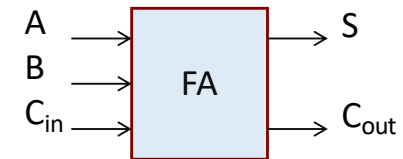




$$S = A'.B'.C_{in} + A'.B.C_{in}' + A.B'C_{in}' + A.B.C$$

$$= A \oplus B \oplus C_{in}$$

$$C_{out} = B.C_{in} + A.C_{in} + A.B + A.B.C_{in}$$

$$= A.B + B.C_{in} + A.C_{in}$$


Various Implementations of Full Adder

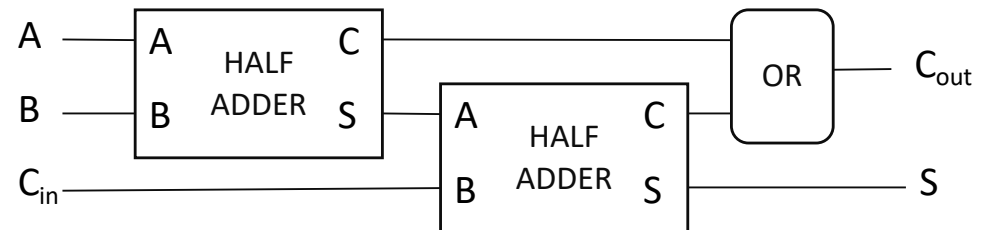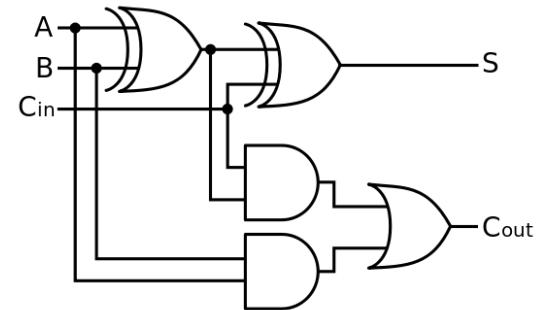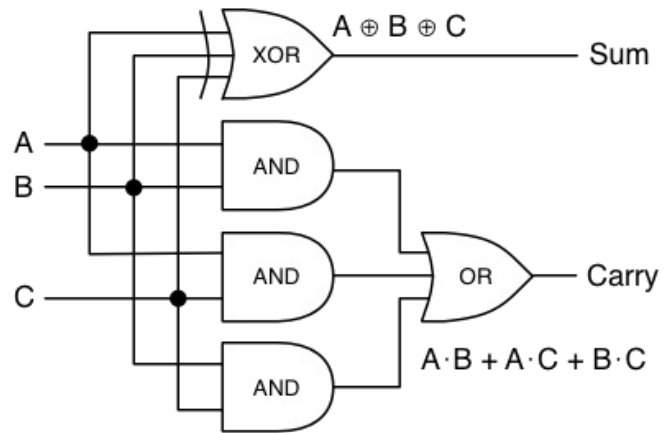

8

- **Delay of a full adder:**

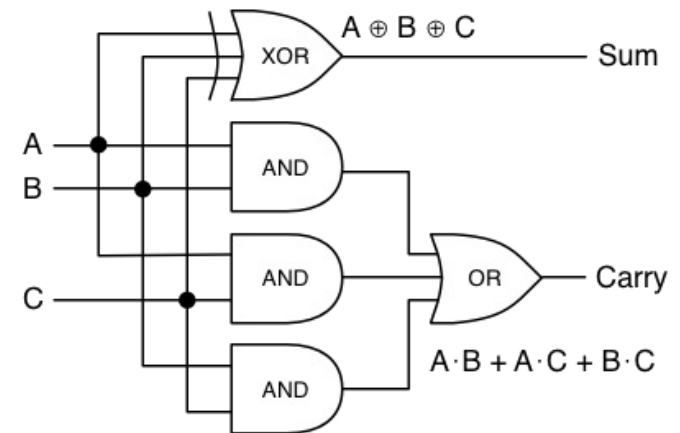- Assume that the delay of all basic gates (AND, OR, NAND, NOR, NOT) is δ
- Delay for Carry = 2δ
- Delay for Sum = 3δ
(AND-OR delay plus one inverter delay)




Parallel Adder Design

- We shall look at the various designs of n -bit parallel adder.
 - a) Ripple carry adder
 - b) Carry look-ahead adder
 - c) Carry save adder
 - d) Carry select adder

Ripple Carry Adder

- Cascade n full adders to create a n -bit parallel adder.
- Carry output from stage- i propagates as the carry input to stage- $(i+1)$.
- In the worst-case, carry ripples through all the stages.

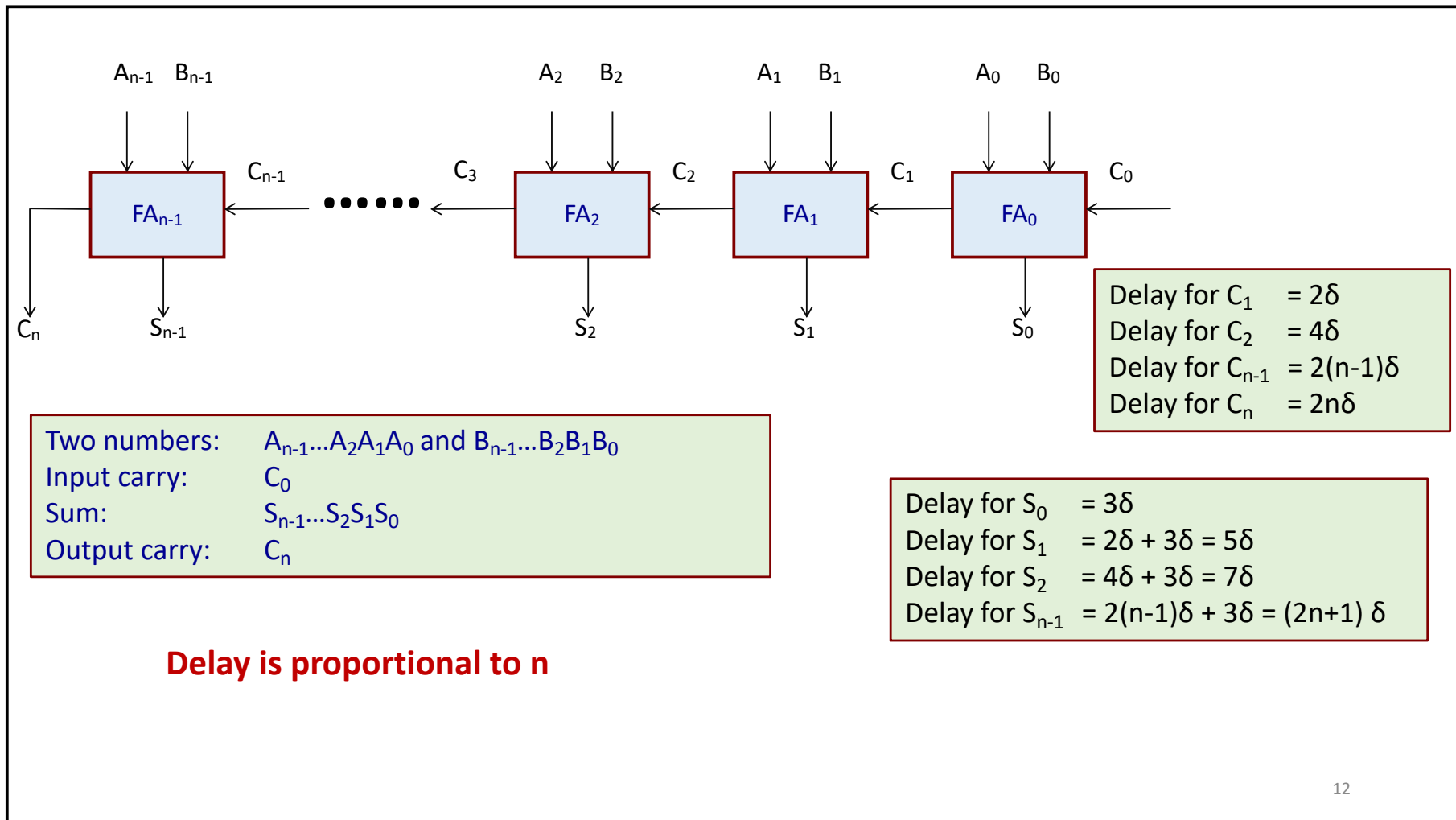
$$\begin{array}{r}
 1\ 1\ 1\ 1\ 1\ 1\ 0 \leftarrow \text{Carry} \\
 0\ 1\ 1\ 1\ 1\ 1\ 1 \leftarrow \text{Number A} \\
 +\ 0\ 0\ 0\ 0\ 0\ 0\ 1 \leftarrow \text{Number B} \\
 \hline
 1\ 0\ 0\ 0\ 0\ 0\ 0 \leftarrow \text{Sum S}
 \end{array}$$




How to Design a Parallel Subtractor?

- **Observation:**

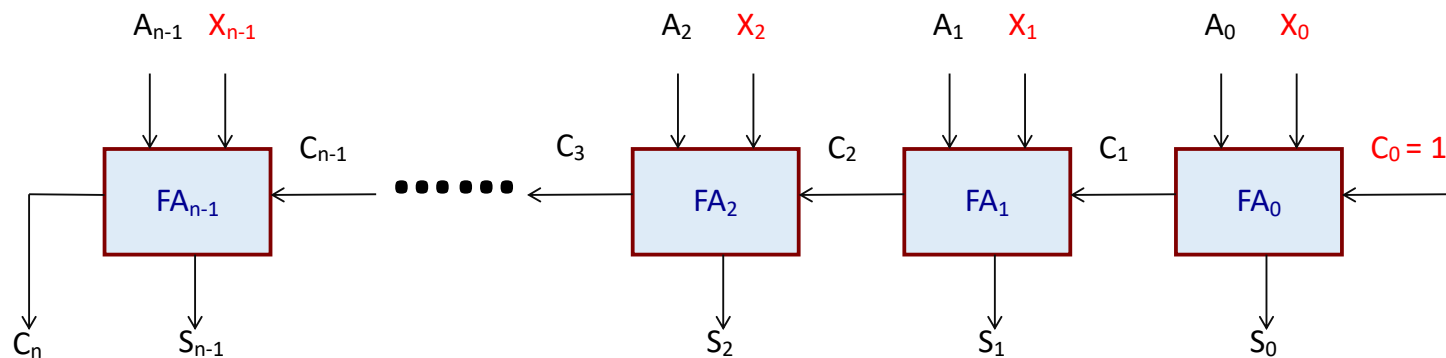- Computing $A - B$ is the same as adding the 2's complement of B to A .
- 2's complement is equal to 1's complement plus 1.
- Let $X_i = B_i'$.



A Parallel Adder/Subtractor

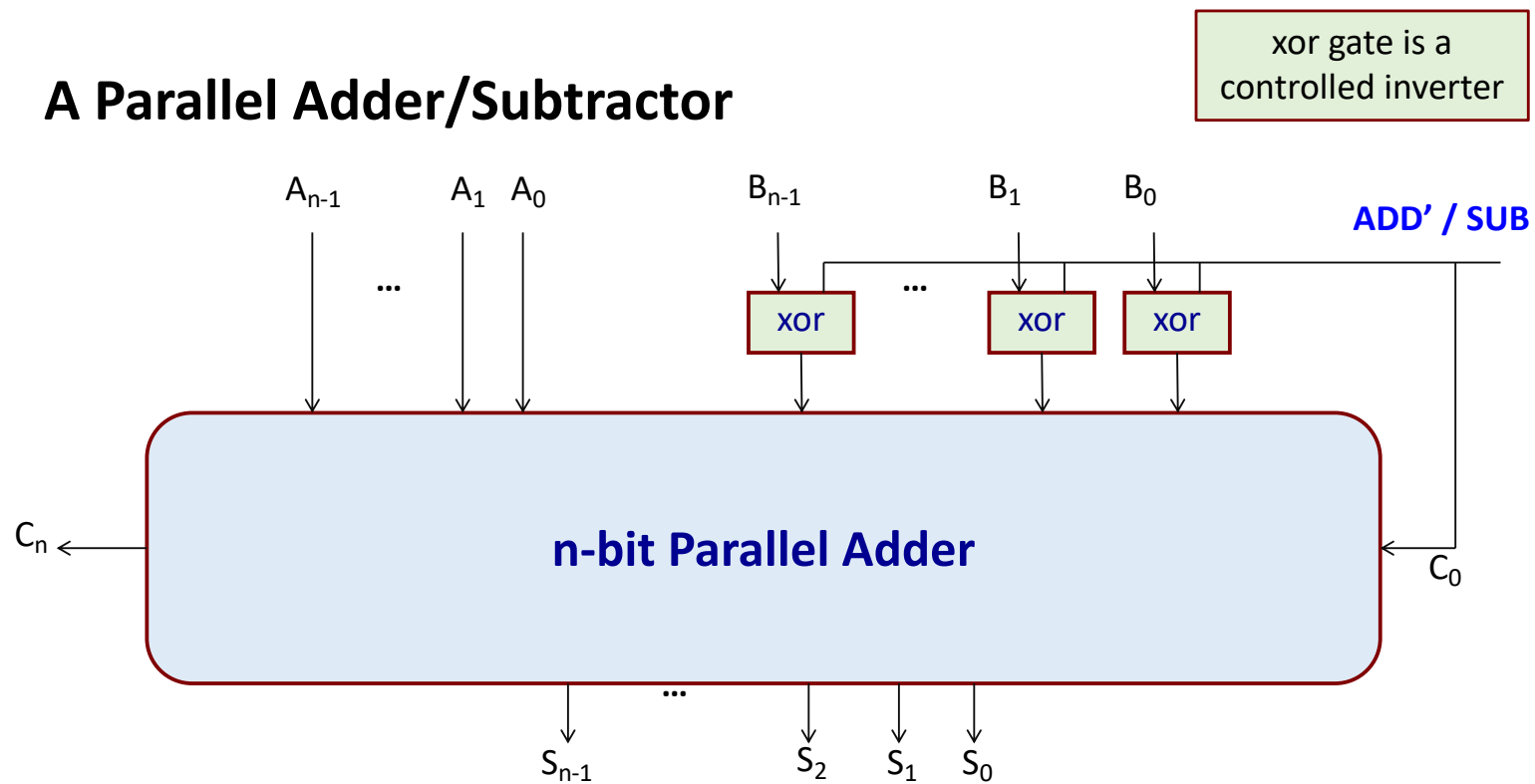

14

Carry Look-ahead Adder


- The propagation delay of an n -bit ripple carry order has been seen to be proportional to n .
 - Due to the rippling effect of carry sequentially from one stage to the next.
- One possible way to speedup the addition.
 - Generate the carry signals for the various stages in parallel.
 - Time complexity reduces from $O(n)$ to $O(1)$.
 - However, hardware complexity increases rapidly with n .

- Consider the i -th stage in the addition process.
- We define the *carry generate* and *carry propagate* functions as:

$$G_i = A_i \cdot B_i$$

$$P_i = A_i \oplus B_i$$

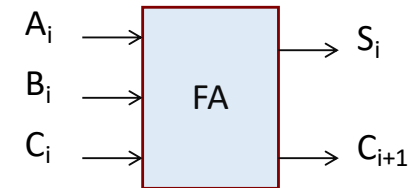- $G_i = 1$ represents the condition when a carry is generated in stage- i independent of the other stages.
- $P_i = 1$ represents the condition when an input carry C_i will be propagated to the output carry C_{i+1} .



$$C_{i+1} = G_i + P_i \cdot C_i$$

16

Unrolling the Recurrence

$$\begin{aligned}
 C_{i+1} &= G_i + P_i C_i = G_i + P_i (G_{i-1} + P_{i-1} C_{i-1}) = G_i + P_i G_{i-1} + P_i P_{i-1} C_{i-1} \\
 &= G_i + P_i G_{i-1} + P_i P_{i-1} (G_{i-2} + P_{i-2} C_{i-2}) \\
 &= G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + P_i P_{i-1} P_{i-2} C_{i-2} = \dots
 \end{aligned}$$

$$C_{i+1} = G_i + \sum_{k=0}^{i-1} G_k \prod_{j=k+1}^i P_j + C_0 \prod_{j=0}^i P_j$$

Design of 4-bit CLA Adder

$$C_4 = G_3 + G_2P_3 + G_1P_2P_3 + G_0P_1P_2P_3 + C_0P_0P_1P_2P_3$$

$$C_3 = G_2 + G_1P_2 + G_0P_1P_2 + C_0P_0P_1P_2$$

$$C_2 = G_1 + G_0P_1 + C_0P_0P_1$$

$$C_1 = G_0 + C_0P_0$$

$$S_0 = A_0 \oplus B_0 \oplus C_0 = P_0 \oplus C_0$$

$$S_1 = P_1 \oplus C_1$$

$$S_2 = P_2 \oplus C_2$$

$$S_3 = P_3 \oplus C_3$$

4 AND2 gates
3 AND3 gates
2 AND4 gates
1 AND5 gate
1 OR2, 1 OR3, 1 OR4 and
1 OR5 gate

4 XOR2 gates

18

Design of 4-bit CLA Adder

$$C_4 = G_3 + G_2P_3 + G_1P_2P_3 + G_0P_1P_2P_3 + C_0P_0P_1P_2P_3$$

$$C_3 = G_2 + G_1P_2 + G_0P_1P_2 + C_0P_0P_1P_2$$

$$C_2 = G_1 + G_0P_1 + C_0P_0P_1$$

$$C_1 = G_0 + C_0P_0$$

$$S_0 = A_0 \oplus B_0 \oplus C_0 = P_0 \oplus C_0$$

$$S_1 = P_1 \oplus C_1$$

$$S_2 = P_2 \oplus C_2$$

$$S_3 = P_3 \oplus C_3$$

4 AND2 gates
 3 AND3 gates
 2 AND4 gates
 1 AND5 gate
 1 OR2, 1 OR3, 1 OR4 and
 1 OR5 gate

4 XOR2 gates

Design of 4-bit CLA Adder

$$C_4 = G_3 + \mathbf{C_3}P_3$$

$$C_3 = G_2 + G_1P_2 + G_0P_1P_2 + C_0P_0P_1P_2$$

$$C_2 = G_1 + G_0P_1 + C_0P_0P_1$$

$$C_1 = G_0 + C_0P_0$$

$$S_0 = A_0 \oplus B_0 \oplus C_0 = P_0 \oplus C_0$$

$$S_1 = P_1 \oplus C_1$$

$$S_2 = P_2 \oplus C_2$$

$$S_3 = P_3 \oplus C_3$$

4 AND2 gates

2 AND3 gates

1 AND4 gates

~~1~~ AND5-gate


1 OR2, 1 OR3, 1 OR4 and


1 **OR2** gate

4 XOR2 gates


20

The 4-bit CLA Circuit

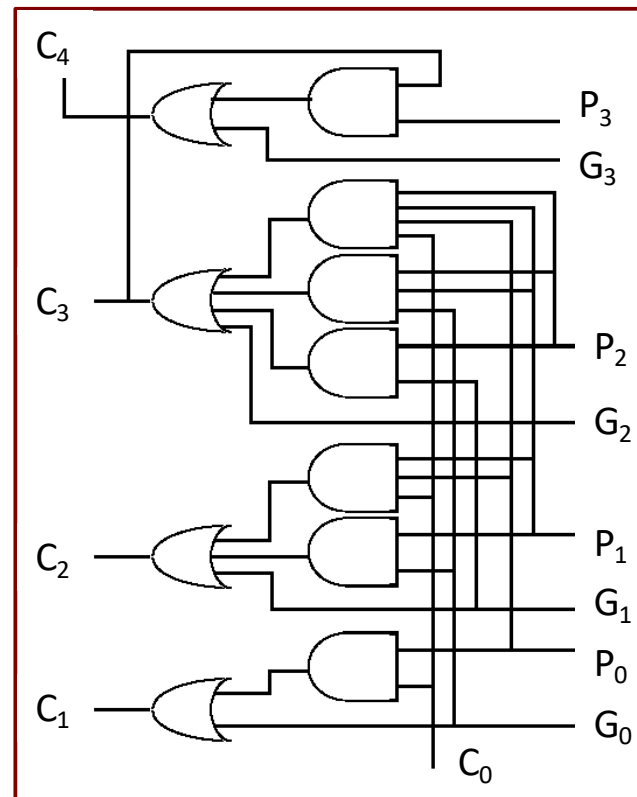

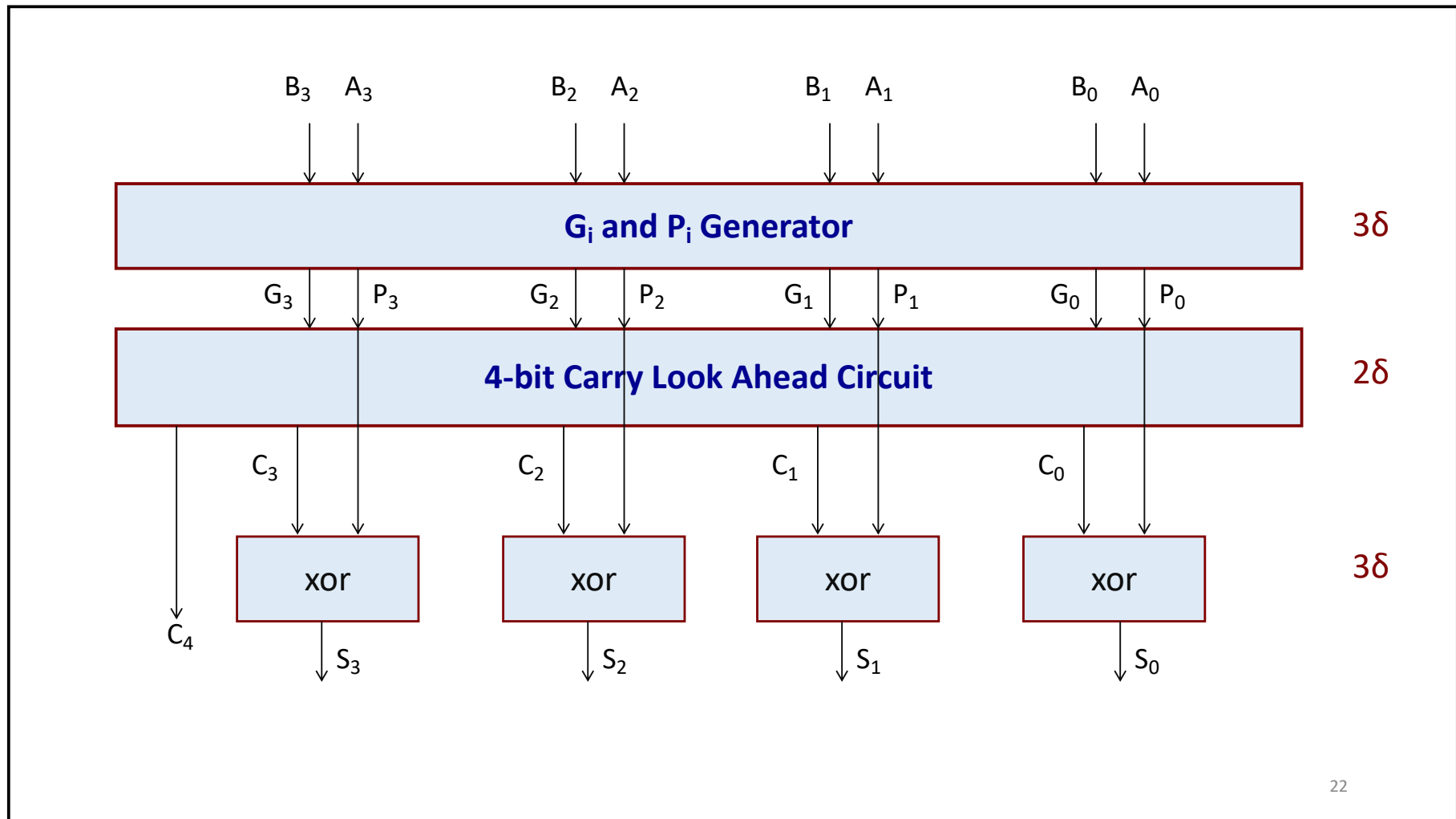

16-bit Adder Using 4-bit CLA Modules

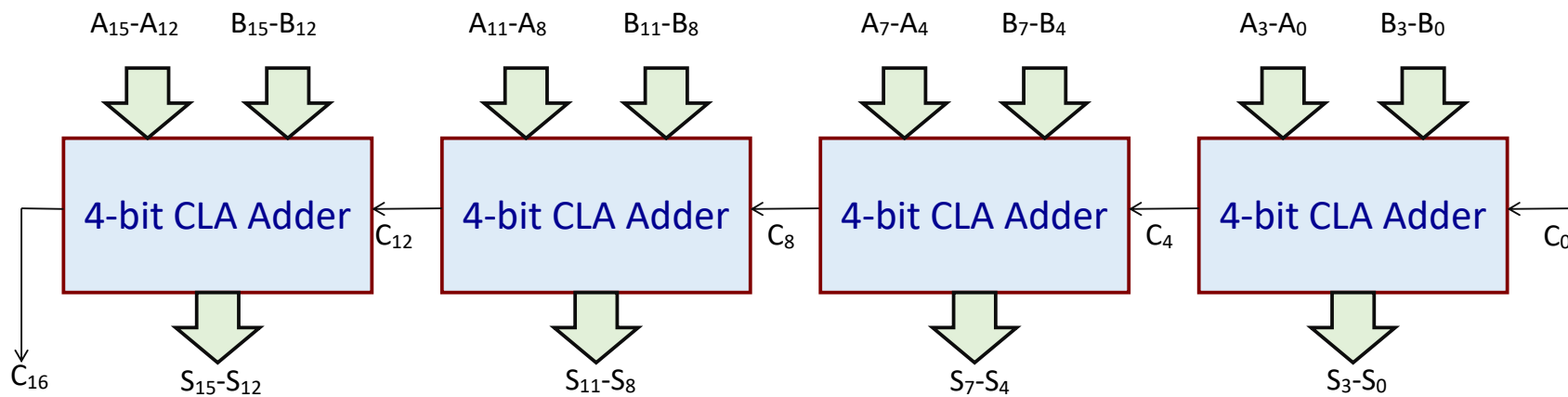

Problem: Carry propagation between modules still slows down the adder

- **Solution:**

- Use a second level of carry look-ahead mechanism to generate the input carries to the CLA blocks in parallel.
- The second level of CLA generates C4, C8, C12 and C16 in parallel with two gate delays (2δ).
- For larger values of n , more CLA levels can be added.
- Delay calculation of a 16-bit adder:
 - a) For original single-level CLA: 14δ
 - b) For modified two-level CLA: 10δ

24

Delay of a k-bit Adder

n	T_{CLA}	T_{RCA}
4	8δ	9δ
16	10δ	33δ
32	12δ	65δ
64	12δ	129δ
128	14δ	257δ
256	14δ	513δ

$$T_{CLA} = (6 + 2\lceil \log_4 n \rceil) \delta$$

$$T_{RCA} = (2n + 1) \delta$$


Carry Select Adder

- Basically consists of two parallel adders (say, ripple-carry adder) and a multiplexer.
- For two given numbers A and B , we carry out addition twice:
 - With carry-in as 0
 - With carry-in as 1
- Once the correct carry-in is known, the correct sum is selected by a multiplexer.

26


Basic building block of a carry-select adder, with block size of 4.

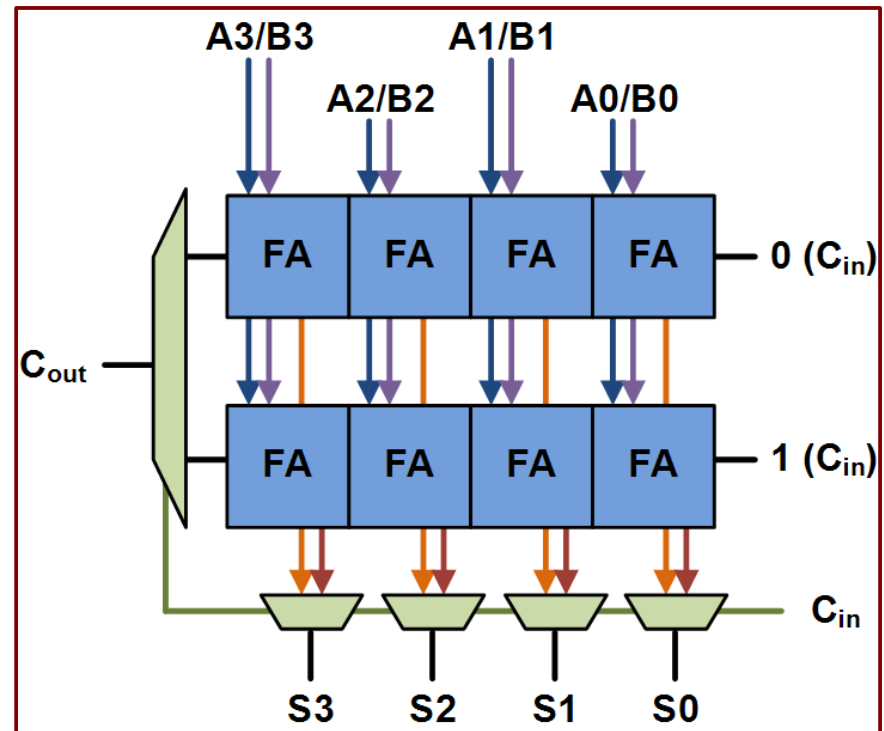- For a multi-bit adder, the number of bits in each carry select block can be either uniform or variable.



Uniform sized adder

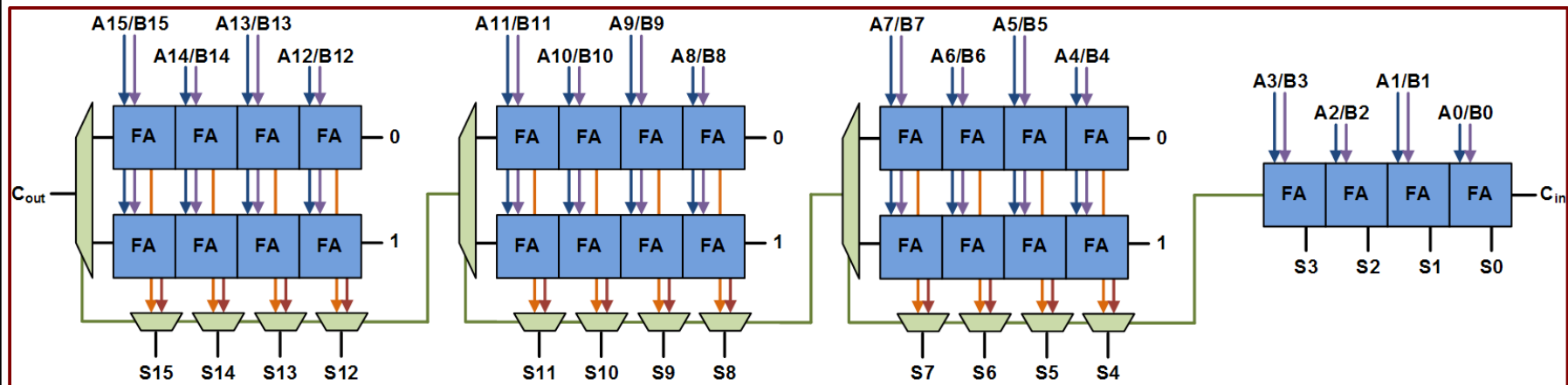
- A 16-bit carry select adder with a uniform block size of 4 is shown.
- The least significant block needs a single adder (since the carry-in is known).
- Total delay is 4 full adder delays, plus 3 MUX delays.



28

Variable-sized adder

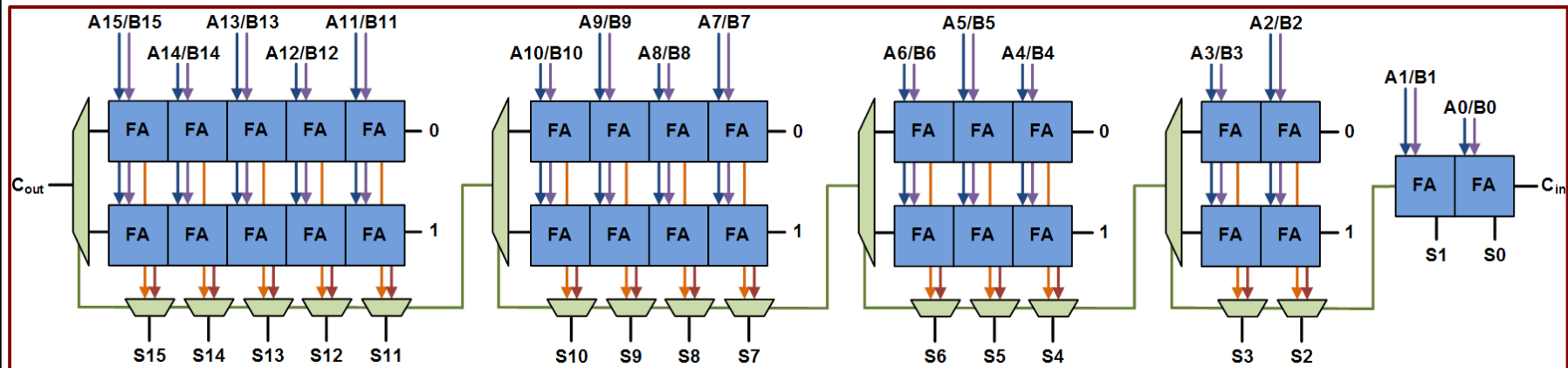- A 16-bit carry select adder with variable block sizes of 2-2-3-4-5 is shown.
- Total delay is 2 full adder delays, plus 4 MUX delays.



Carry Save Adder

- Here we add three operands (say, X , Y and Z) together.
- For adding multiple numbers, we have to construct a tree of carry save adders.
 - Used in combinational multiplier design.
- Each carry save adder is simply an independent full adder without carry propagation.
- A parallel adder is required only at the last stage.

30

- An illustrative example:

$$\begin{array}{r}
 X: \quad 10011 \\
 Y: + 11001 \\
 Z: + 01011 \\
 \hline
 C: \quad 11011
 \end{array}$$


$$\begin{array}{r}
 X: \quad 10011 \\
 Y: + 11001 \\
 Z: + 01011 \\
 \hline
 S: \quad 00001
 \end{array}$$

A set of full adders generate carry
and sum bits in parallel

$$\begin{array}{r}
 X: \quad 10011 \\
 Y: + 11001 \\
 Z: + 01011 \\
 \hline
 S: \quad 00001 \\
 C: \quad 11011 \\
 \hline
 \text{Sum: } 110111
 \end{array}$$

The sum and carry vectors are
added later (with proper shifting)




An n-bit Carry Save Adder

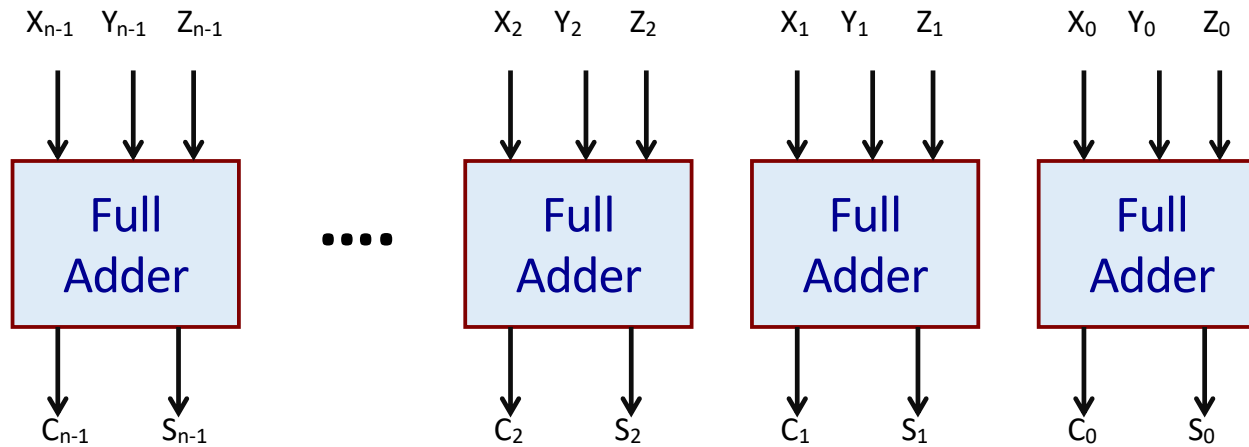

The carry input of the full adder is used as the third input

32


Adding m Numbers: Some Examples

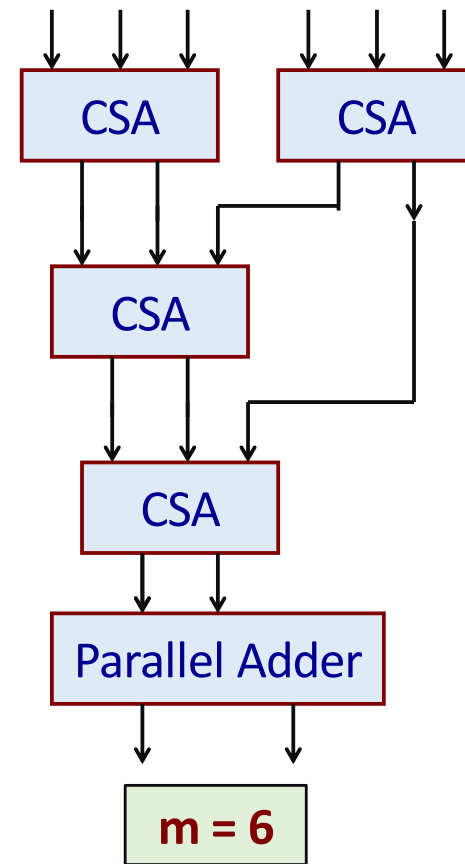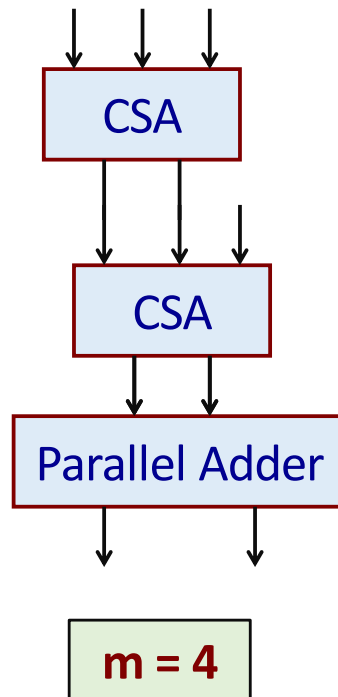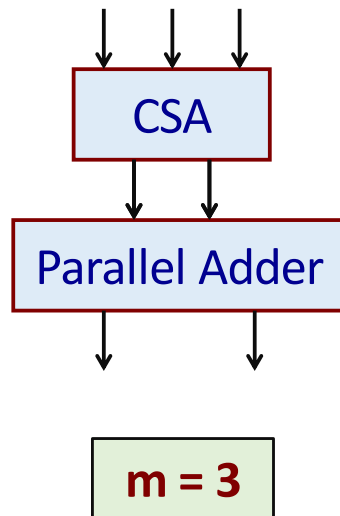



Generating the Status Flags

- Many contemporary processors have a *flag register* that contains the status of the last arithmetic / logic operation.
 - **Zero (Z)**: tells whether the result is zero.
 - Can be used for both arithmetic and logic operations.
 - **Sign (S)**: tells whether the result is positive (=0) or negative (=1).
 - Can be used for both arithmetic and logic operations.
 - **Carry (C)**: tells whether there has been a carry out of the most significant stage.
 - Used only for arithmetic operations.
 - **Overflow (V)**: tells whether the result is too large to fit in the target register.
 - Used only for arithmetic operations (addition and subtraction).

34

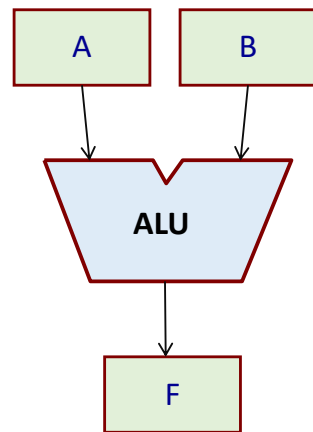

Assume A , B and F are n -bit registers

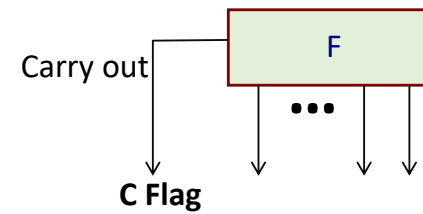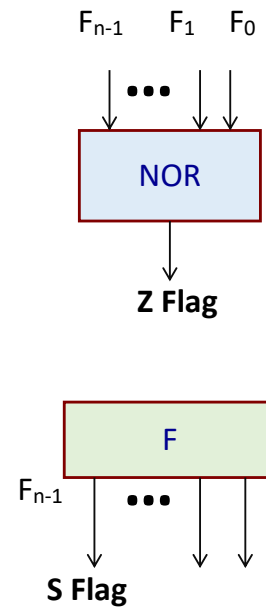

- Overflow can occur during addition when the sign of the two operands are the same.

- Sign of the result becomes different from the sign of the operand(s).

$$V = A_{n-1} \cdot B_{n-1} \cdot F_{n-1}' + A_{n-1}' \cdot B_{n-1}' \cdot F_{n-1}$$

$$V = F_{n-1} \oplus \text{Carry_out}$$

- The MIPS32 processor does not have any status flags.
- Why?
 - MIPS ISA is designed for efficient pipeline implementation.
 - Several instructions can be in various stages of execution in the pipeline.
 - Flag registers result in *side effects* among instructions.
- MIPS stores information about the flags temporarily in a GPR.

```
slt    $t0,$s1,$s2  
beq    $t0,$zero,Label
```

36